

Exercise 1:

■ The simplified functions (Circuit 1)

- ◆ $z = D'$
- ◆ $y = CD + C'D'$
- ◆ $x = B'C + B'D + BC'D'$
- ◆ $w = A + BC + BD$

■ Another implementation (Circuit 2)

- ◆ $z = D'$
- ◆ $y = CD + C'D' = CD + (C+D)'$
- ◆ $x = B'C + B'D + BC'D' = B'(C+D) + B(C+D)'$
- ◆ $w = A + BC + BD = A + B(C+D)$

■ Draw the logic diagrams of Circuit 1 and Circuit 2, and then verify Circuit 1 = Circuit 2 (using Verilog Dataflow modeling)

Exercise 2:

■ Derive the following Boolean functions using Karnaugh maps

■ $S = z \oplus (x \oplus y)$, $C = xy + xz + yz$ (Circuit 1)

■ Draw the logic diagram of Circuit 1

■ Derive the following Boolean functions using Karnaugh maps

■ $S = z \oplus (x \oplus y)$, $C = z(x \oplus y) + xy$ (Circuit 2)

■ Draw the logic diagram of Circuit 2

■ Verify Circuit 1 = Circuit 2 (using Verilog Structural level modeling)

Exercise 3:

■ Design and verify the 8-bit ripple-carry adder composed of eight full-adders (using Verilog Structural level modeling)

實驗內容

一、Exercise 1:

■ The simplified functions (Circuit 1)


- ◆ $z = D'$
- ◆ $y = CD + C'D'$
- ◆ $x = B'C + B'D + BC'D'$
- ◆ $w = A + BC + BD$

■ Another implementation (Circuit 2)


- ◆ $z = D'$
- ◆ $y = CD + C'D' = CD + (C+D)'$
- ◆ $x = B'C + B'D + BC'D' = B'(C+D) + B(C+D)'$
- ◆ $w = A + BC + BD = A + B(C+D)$

■ Draw the logic diagrams of Circuit 1 and Circuit 2, and then verify Circuit 1 = Circuit 2 (using Verilog Dataflow modeling)

Circuit 1 :

 

Circuit 2 :

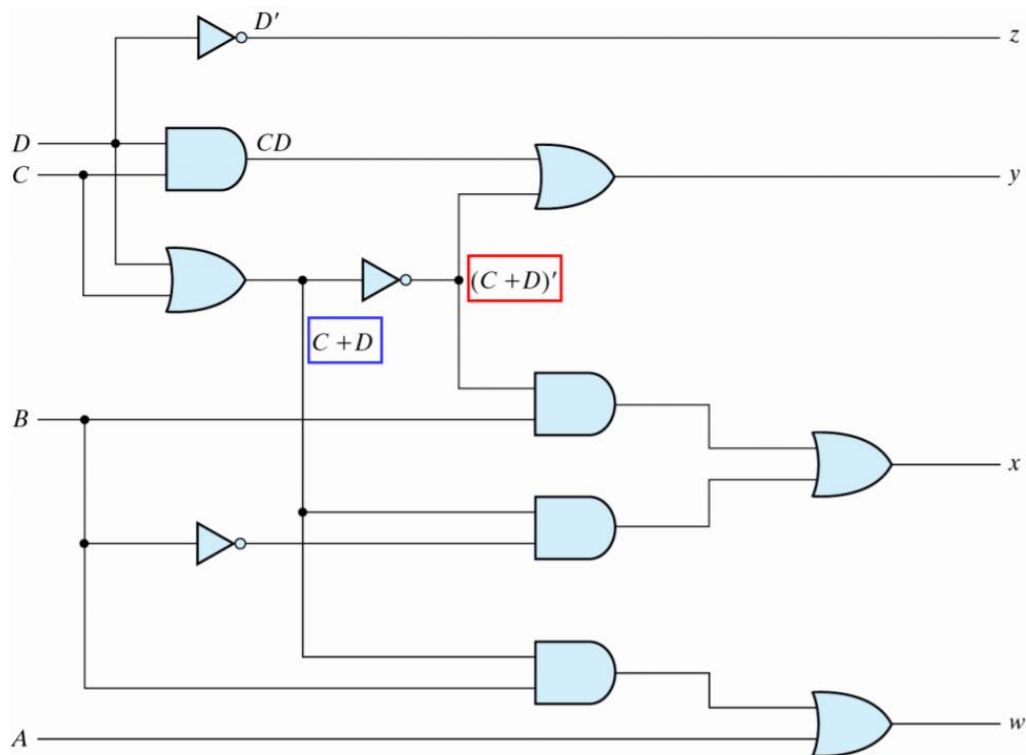


```

1      *timescale 1ns / 1ps
2
3      module exercise_1(w,x,y,z,w2,x2,y2,z2, A,B,C,D);
4          output w,x,y,z,w2,x2,y2,z2;
5          input A,B,C,D;
6          assign z = ~D;
7          assign y = (C & D) | (~C & ~D);
8          assign x = (~B & C) | (~B & D) | (B & ~C & ~D);
9          assign w = A | (B & C) | (B & D);
10
11         assign z2 = ~D;
12         assign y2 = (C & D) | ~(C | D);
13         assign x2 = (~B & (C | D)) | (B & ~(C | D));
14         assign w2 = A | (B & (C | D));
15     endmodule
16

```

 
Circuit 2 中將(C+D)都提出來，在 Schematic 中可以使成本節省，體積變小



$w=w2, x=x2, y=y2, z=z2$, 所以 Circuit 1= Curcuit 2


二、Exercise 2:

 - Derive the following Boolean functions using Karnaugh maps
- $S = z \oplus (x \oplus y)$, $C = xy + xz + yz$ (Circuit 1)
- Draw the logic diagram of Circuit 1



這是一般的 Karnaugh maps 化簡。

 - Derive the following Boolean functions using Karnaugh maps
- $S = z \oplus (x \oplus y)$, $C = z(x \oplus y) + xy$ (Circuit 2)
- Draw the logic diagram of Circuit 2
- Verify Circuit 1 = Circuit 2
(using Verilog Structural level modeling)




因為 $(x \oplus y)$ 在 S 就已經出現了，可以節省電晶體，但延遲會多一點。

程式如右:

```

1      ~timescale 1ns / 1ps
2
3      module exercise_2(S1,C1,S2,C2,x,y,z);
4          output S1,C1,S2,C2;
5          input x,y,z;
6          wire n1,n2,n3,n4,n5,n6,n7;
7
8
9      ○   xor(n1,x,y);
10     ○   xor(S1,z,n1);
11
12     ○   and(n2,x,y);
13     ○   and(n3,x,z);
14     ○   and(n4,z,y);
15     ○   or(C1,n2,n3,n4);
16
17     ○   buf(S2,S1);
18     ○   and(n5,z,n1);
19     ○   or(C2,n2,n5);
20     endmodule
21

```

 

由電壓圖 S1=S2 , C1=C2(上到下: 輸入:x,y,z 輸出:S1,C1;S2,C2)

三、Exercise 3:

- Design and verify the 8-bit ripple-carry adder composed of eight full-adders (using Verilog **Structural level modeling**)

```

1 | ~timescale 1ns / 1ps
2 |
3 | module half_adder (output S,C,input x,y);
4 |     xor(S,x,y);
5 |     and(C,x,y);
6 | endmodule
7 |
8 | module full_adder (output S,C,input x,y,z);
9 |     wire S1,C1,C2;
10 |
11 |     half_adder HA1(S1,C1,x,y);
12 |     half_adder HA2(S,C2,S1,z);
13 |     or(C,C2,C1);
14 | endmodule
15 |
16 |
17 | module exercise_3(output [7:0]S, output C8, input [7:0]A,B,input C0);
18 |     wire C1,C2,C3,C4,C5,C6,C7;
19 |
20 |     full_adder FA0(S[0],C1,A[0],B[0],C0),
21 |     FA1(S[1],C2,A[1],B[1],C1),
22 |     FA2(S[2],C3,A[2],B[2],C2),
23 |     FA3(S[3],C4,A[3],B[3],C3),
24 |     FA4(S[4],C5,A[4],B[4],C4),
25 |     FA5(S[5],C6,A[5],B[5],C5),
26 |     FA6(S[6],C7,A[6],B[6],C6),
27 |     FA7(S[7],C8,A[7],B[7],C7);
28 | endmodule
29 |

```


程式碼如右：


(1) half_adder :

(2) full_adder :


含 2 個半加器與 1 個 OR 閘

(3) 將 8 個全加器接在一起就是 8_bit 加法器

 

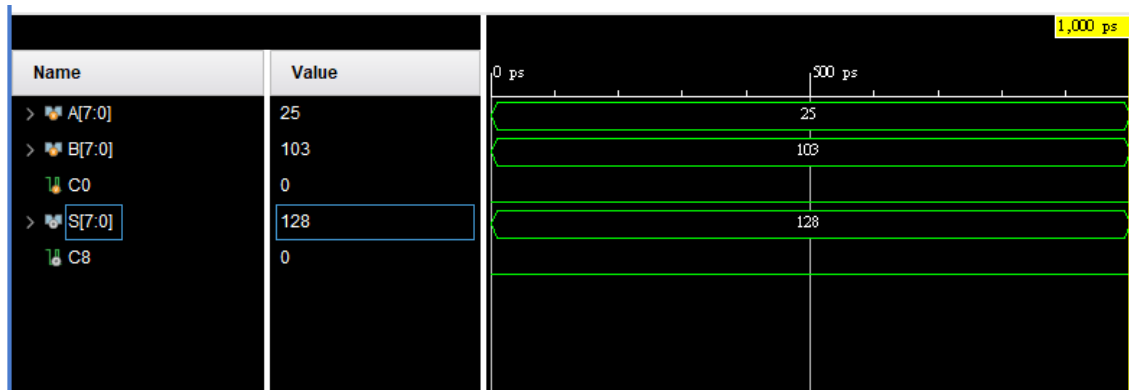

由電壓圖 $[7:0]A + [7:0]B = [7:0]S$

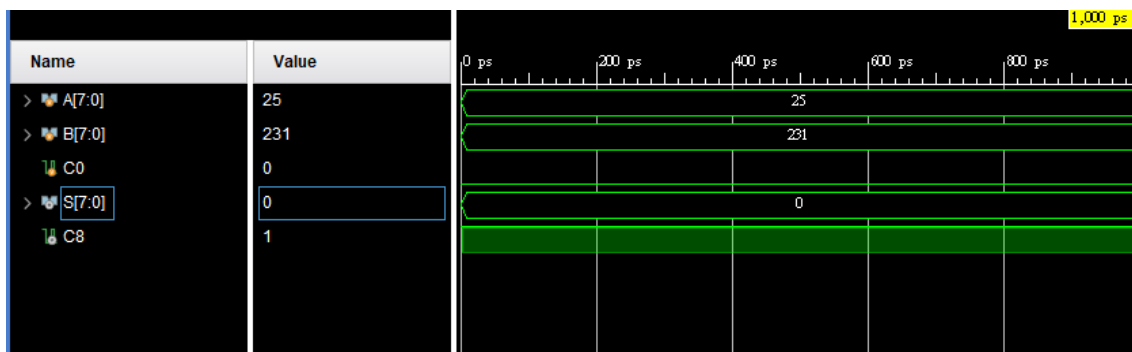

由電壓圖 $[7:0]A + [7:0]B = [7:0]S$ ，S 無法顯示大於(含) 2^8 ->也就是 S 只能 <256
 若 $S > 256$ ，則 C8 輸出 1；

實驗心得

1. Structural level modeling 中邏輯閘使用函數表示
 2. Structural level modeling 可以很直觀的轉換成 Schematic
 3. Structural level modeling 需要宣告邏輯閘之間的線路
 4. 所有的 modeling 都需要注意該邏輯閘是否有交換律或結合律
 5. Exercise 1 的 don't care conditions 很好用可以簡化電路
 6. Exercise 2、3、4 電路的轉換用 Schematic 畫出來後比較簡單。
- 例如:exercise2:AND-OR gate 轉成 multi-level NAND gate、multi-level NOR gate.....。