

Exercise 1:

***Exercise 1: 3-to-8 Decoder (1/2)***

- Design and verify a 3-to-8 decoder composed of two 2-to-4 decoders

<i>A</i>	<i>B</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>
0	0	<i>E</i>	0	0	0
0	1	0	<i>E</i>	0	0
1	0	0	0	<i>E</i>	0
1	1	0	0	0	<i>E</i>

<i>E</i>	<i>A</i>	<i>B</i>	<i>D</i> <sub>0</sub>	<i>D</i> <sub>1</sub>	<i>D</i> <sub>2</sub>	<i>D</i> <sub>3</sub>
0	<i>X</i>	<i>X</i>	0	0	0	0
1	0	0	1	0	0	0
1	0	1	0	1	0	0
1	1	0	0	0	1	0
1	1	1	0	0	0	1

Exercise 2:

***Exercise 2: 8-to-1 Multiplexer (1/2)***

- Design and verify the 8-to-1 multiplexer composed of a 3×8 decoder and three-state gates using Verilog HDL
- ◆ Structural level (Gate-level) modeling

Exercise 3:

### ***Exercise 3: Boolean Function Implementation (1/2)***

- Design and verify the 8-to-1 multiplexer using Verilog HDL
  - ◆ Behavioral level modeling
- Implement and verify the following Boolean function of 4 input variable using 8-to-1 MUX
  - ◆  $F(A, B, C, D) = \Sigma(1, 2, 5, 8, 9, 10, 12, 13)$

# 實驗內容

## 一、Exercise 1:

### Exercise 1: 3-to-8 Decoder (1/2)

■ Design and verify a 3-to-8 decoder composed of two 2-to-4 decoders

3x8 decoder 用 2 個 2x4

decoder 接


2x4 decoder =

$\Sigma(1,2,3,4)$

```
timescale 1ns / 1ps

module decoder_2x4_gates (D, A, B, enable);
    output [3: 0] D;
    input A, B;
    input enable;
    wire A_not, B_not, enable_not;
    not (A_not, A);
    not (B_not, B);
    not (enable_not, enable);
    and (D[0], A_not, B_not, enable);
    and (D[1], A_not, B, enable);
    and (D[2], A, B_not, enable);
    and (D[3], A, B, enable);
endmodule

 module exercise_1 (D, x, y, z);
    output [7: 0] D;
    input x, y, z;
    decoder_2x4_gates D03(D[3:0], y, z, ~x);
    decoder_2x4_gates D47(D[7:4], y, z, x);
endmodule
```



## 二、Exercise 2:

### Exercise 2: 8-to-1 Multiplexer (1/2)

- Design and verify the 8-to-1 multiplexer composed of a 3×8 decoder and three-state gates using Verilog HDL


- ◆ Structural level (Gate-level) modeling

```
1      timescale 1ns / 1ps
2      module decoder_2x4_gates (D, A, B, enable);
3          output [3: 0] D;
4          input A, B;
5          input enable;
6          wire A_not, B_not, enable_not;
7          not (A_not, A);
8          not (B_not, B);
9          not (enable_not, enable);
10         and (D[0], A_not, B_not, enable);
11         and (D[1], A_not, B, enable);
12         and (D[2], A, B_not, enable);
13         and (D[3], A, B, enable);
14     endmodule
15
16     module decoder_3x8_df (D, x, y, z);
17         output [7:0] D;
18         input x, y, z;
19         decoder_2x4_gates D03(D[3:0], z, y, ~x);
20         decoder_2x4_gates D47(D[7:4], z, y, x);
21     endmodule
22
23     module exercise_2 (Y, I0, I1, I2, I3, I4, I5, I6, I7, S0, S1, enable);
24         output Y;
25         input I0, I1, I2, I3, I4, I5, I6, I7, S0, S1, enable;
26         tri Y;
27         wire [7: 0] D;
28         decoder_3x8_df D03(D[7:0], S0, S1, enable);
29         bufif1(Y, I0, D[0]);
30         bufif1(Y, I1, D[1]);
31         bufif1(Y, I2, D[2]);
32         bufif1(Y, I3, D[3]);
33         bufif1(Y, I4, D[4]);
34         bufif1(Y, I5, D[5]);
35         bufif1(Y, I6, D[6]);
36         bufif1(Y, I7, D[7]);
37     endmodule
38
```

8bit MUX 拆成 3x8 decoder + three-state gates ,

3x8 decoder 拆成 2 個 2x4 decoder

2x4 decoder =  $\Sigma(1,2,3,4)$

 


$$Y = I_0 > I_1 > I_2 > I_3 > I_4 > I_5 > I_6 > I_7$$


### 三、Exercise 3:

#### Exercise 3: Boolean Function Implementation (1/2)

- Design and verify the 8-to-1 multiplexer using Verilog HDL
  - ◆ Behavioral level modeling
- Implement and verify the following Boolean function of 4 input variable using 8-to-1 MUX
  - ◆  $F(A, B, C, D) = \Sigma(1, 2, 5, 8, 9, 10, 12, 13)$

A	B	C	D	F	
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	1	$F = D'$
0	0	1	1	0	
0	1	0	0	0	$F = D$
0	1	0	1	1	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	1	$F = 1$
1	0	0	1	1	
1	0	1	0	1	$F = D'$
1	0	1	1	0	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	0	$F = 0$
1	1	1	1	0	

 

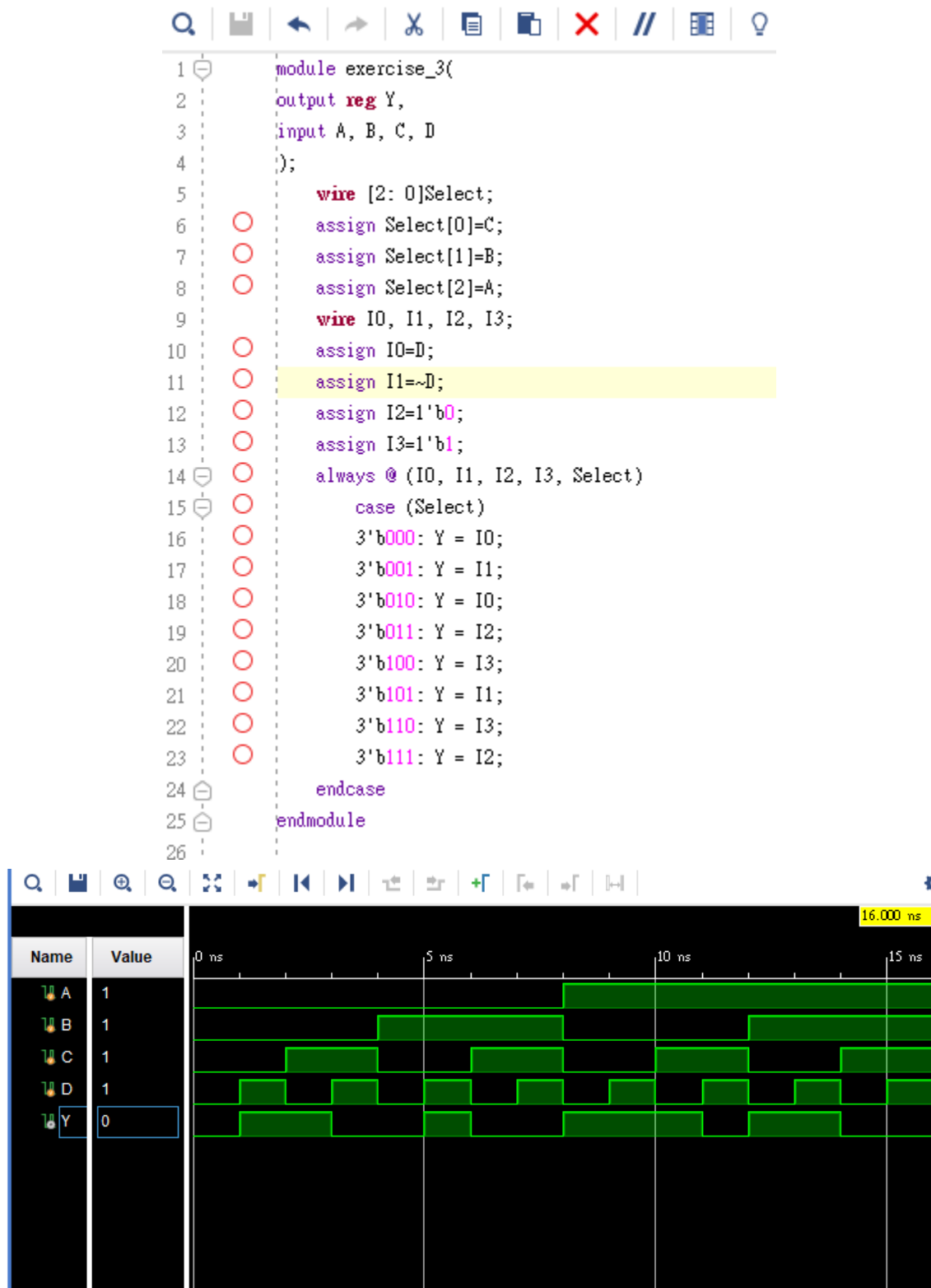

$$Y = \Sigma(1,2,3,5,8,9,10,12,13)$$

# 實驗心得

1. Structural level modeling 中邏輯閘使用函數表示
2. Structural level modeling 可以很直觀的轉換成 Schematic
3. Structural level modeling 需要宣告邏輯閘之間的線路
4. 所有的 modeling 都需要注意該邏輯閘是否有交換律或結合律