

## Exercise 1:

## ■ Nine's Complement Converter

Digits		Nine's Complements	
Decimal	BCD	Decimal	BCD
	$x_3 x_2 x_1 x_0$		$y_3 y_2 y_1 y_0$
0	0 0 0 0	9	1 0 0 1
1	0 0 0 1	8	1 0 0 0
2	0 0 1 0	7	0 1 1 1
3	0 0 1 1	6	0 1 1 0
4	0 1 0 0	5	0 1 0 1
5	0 1 0 1	4	0 1 0 0
6	0 1 1 0	3	0 0 1 1
7	0 1 1 1	2	0 0 1 0
8	1 0 0 0	1	0 0 0 1
9	1 0 0 1	0	0 0 0 0

- Design the nine's complement converter using Karnaugh maps and don't-care conditions, draw the **logic diagram** of the nine's complement converter and verify the circuit (using **Verilog Structural level modeling**)

## Exercise 2:

- $F = (AB' + A'B)(C + D')$
- ◆ Implement  $F$  with **AND-OR gates** (denoted as  $F1$ )
  - ◆ Implement  $F$  with **multi-level NAND gate circuit** (denoted as  $F2$ )
  - ◆ Implement  $F$  with **multi-level NOR gate circuit** (denoted as  $F3$ )
  - ◆ Verify  $F1 = F2 = F3$  (using **Verilog Structural level modeling**)

## Exercise 3:

- Simplify the following Boolean function using Karnaugh maps:  
 $F(x,y,z) = \Sigma (1,2,3,4,5,7)$
- Find the simplest sum of products ( $F4$ ) and draw its logic diagram (two-level implementation)
  - ◆ Implement  $F4$  with two-level NAND gate circuit (denoted as  $F5$ )
  - ◆  $F6 = (F4)'$ , implement  $F6$  with two-level OR-NAND (OAI) circuit
  - ◆ Verify  $F4 = F5 = F6$  (using Verilog Structural level modeling)

Exercise 4:

- Simplify the following Boolean function using Karnaugh maps:  
 $F(x,y,z) = \Sigma (1,2,3,4,5,7)$
- Find the simplest product of sums ( $F7$ ) and draw its logic diagram (two-level implementation)
  - ◆ Implement  $F7$  with two-level NOR gate circuit (denoted as  $F8$ )
  - ◆ Implement  $F7$  with two-level AND-NOR (AOI) circuit (denoted as  $F9$ )
  - ◆ Verify  $F7 = F8 = F9$  (using Verilog Structural level modeling)

## 實驗內容

### 一、Exercise 1:

#### ■ Nine's Complement Converter

Digits		Nine's Complements	
Decimal	BCD	Decimal	BCD
	$x_3 x_2 x_1 x_0$		$y_3 y_2 y_1 y_0$
0	0 0 0 0	9	1 0 0 1
1	0 0 0 1	8	1 0 0 0
2	0 0 1 0	7	0 1 1 1
3	0 0 1 1	6	0 1 1 0
4	0 1 0 0	5	0 1 0 1
5	0 1 0 1	4	0 1 0 0
6	0 1 1 0	3	0 0 1 1
7	0 1 1 1	2	0 0 1 0
8	1 0 0 0	1	0 0 0 1
9	1 0 0 1	0	0 0 0 0

- Design the nine's complement converter using Karnaugh maps and don't-care conditions, draw the **logic diagram** of the nine's complement converter and verify the circuit (using **Verilog Structural level modeling**)

$x_1x_0$		00	01	11	10
$x_3x_2$	00	1	1		
	01				
	11	X	X	X	X
	10			X	X

$$y_3 = x'_3 x'_2 x'_1$$

$x_1x_0$		00	01	11	10
$x_3x_2$					
00				1	1
		0	1	3	2
01	1	1			
	4	5	7	6	
11	X	X	X	X	
	12	13	15	14	
10			X	X	
	8	9	11	10	

$$y_2 = x_2 \oplus x_1$$

$x_3x_2 \backslash x_1x_0$		00	01	11	10
00				1	1
01				1	1
11	X	X	X	X	
10			X	X	

$$y_1 = x_1$$

$x_1x_0 \backslash x_3x_2$		$x_1x_0$			
		00	01	11	10
$x_3x_2$	00	1			1
	01	1			1
	11	X	X	X	X
	10	1		X	X

$$y_0 = x'_0$$

因為不可能輸入  $m_{12} \sim m_{16}$ ，所以  $m_{12} \sim m_{16}$  為 don't care

項，don't care 項可以視為 0 亦可視為 1。

## Structural level

modeling 程式如右:

第 13~16 行:


$y_3 = x_1'x_2'x_3'$

$y_2 = x_1'x_2 + x_1x_2' = x_1 \oplus x_2$

$y_1 = x_1$

$y_0 = x_0'$

```
1  *timescale 1ns / 1ps
2  module exercise_1(y3,y2,y1,y0,x3,x2,x1,x0);
3      output y3,y2,y1,y0;
4      input x3,x2,x1,x0;
5      wire not_x3,not_x2,not_x1,not_x0;
6      wire n1,n2,n3,n4,n5,n6;
7
8      not(not_x3,x3);
9      not(not_x2,x2);
10     not(not_x1,x1);
11     not(not_x0,x0);
12
13     and(y3,not_x1,not_x2,not_x3);
14     xor(y2,x2,x1);
15     buf(y1,x1);
16     not(y0,x0);
17 endmodule
18
```

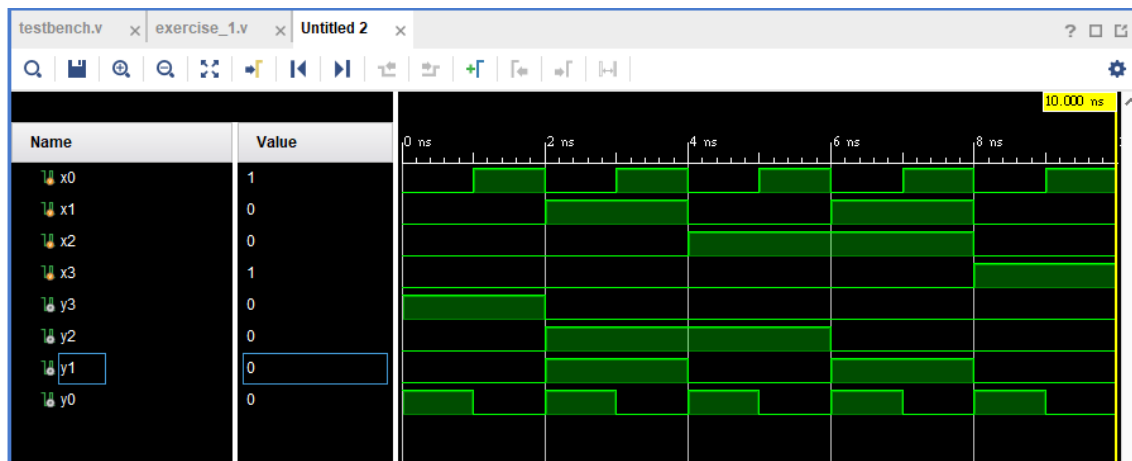

電壓圖完全符合 BCD 碼 9 補數(上到下: 輸入:x0,x1,x2,x3 輸出:y3,y2,y1,y0 )

## 二、Exercise 2:

■  $F = (AB' + A'B)(C + D')$

- ◆ Implement  $F$  with AND-OR gates (denoted as  $F1$ )
- ◆ Implement  $F$  with multi-level NAND gate circuit (denoted as  $F2$ )
- ◆ Implement  $F$  with multi-level NOR gate circuit (denoted as  $F3$ )
- ◆ Verify  $F1 = F2 = F3$  (using Verilog Structural level modeling)

程式如右:

(1)

$$F = (AB' + A'B)(C + D')$$

$$= AB'C + AB'D' + A'BC + A'BD'$$

$$= F1$$

(2)

$$F1 = AB'C + AB'D' + A'BC + A'BD'$$

$$= (AB'C)' + (AB'D')' + (A'BC)' + (A'BD')'$$

$$= (AB'C)'(AB'D')'(A'BC)'(A'BD')'$$

$$= F2$$

(3)

$$F1 = AB'C + AB'D' + A'BC + A'BD'$$

$$= (AB'C)' + (AB'D')' + (A'BC)' + (A'BD')'$$

$$= ((A' + B + C)') + (A' + B + D)' + (A + B' + C')$$


$$+ (A + B'D)')$$

$$= F4$$

```

1      timescale 1ns / 1ps
2
3      module exercise_2(F1,F2,F3,A,B,C,D);
4          output F1,F2,F3;
5          input A,B,C,D;
6          wire not_A,not_B,not_C,not_D;
7          wire n1,n2,n3,n4,n5,n6,n7,n8,n9,n1
8
9          not(not_A,A);
10         not(not_B,B);
11         not(not_C,C);
12         not(not_D,D);
13
14         and(n1,A,not_B,C);
15         and(n2,A,not_B,not_D);
16         and(n3,not_A,B,C);
17         and(n4,not_A,B,not_D);
18         or(F1,n1,n2,n3,n4);
19
20         nand(n5,A,not_B,C);
21         nand(n6,A,not_B,not_D);
22         nand(n7,not_A,B,C);
23         nand(n8,not_A,B,not_D);
24         nand(F2,n5,n6,n7,n8);
25
26         nor(n9,not_A,B,not_C);
27         nor(n10,not_A,B,D);
28         nor(n11,A,not_B,not_C);
29         nor(n12,A,not_B,D);
30         nor(n13,n9,n10,n11,n12);
31         not(F3,n13);
32
33
34     endmodule

```

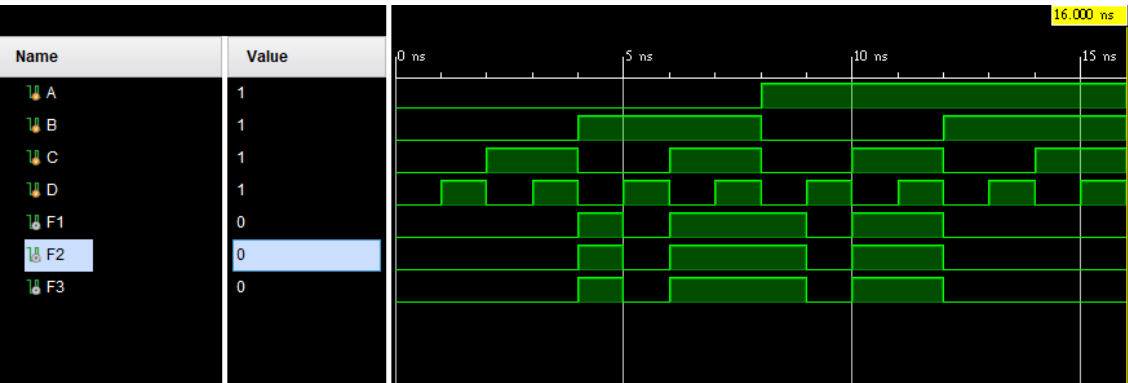

由電壓圖 F1=F2=F3 (上到下：輸入:A,B,C,D 輸出:F1,F2,F3 )




### 三、Exercise 3:

■ Simplify the following Boolean function using Karnaugh maps:  
 $F(x,y,z) = \Sigma (1,2,3,4,5,7)$

■ Find the simplest sum of products ( $F4$ ) and draw its logic diagram (two-level implementation)

 - ◆ Implement  $F4$  with two-level NAND gate circuit (denoted as  $F5$ )
- ◆  $F6 = (F4)'$ , implement  $F6$  with two-level OR-NAND (OAI) circuit
- ◆ Verify  $F4 = F5 = F6$  (using Verilog Structural level modeling)



程式碼如右:

(1)

The simplest sum of products 選越多相鄰越好

$$F4 = x'y + xy' + z$$

(2)

$$\begin{aligned} F4 &= x'y + xy' + z = (x'y)'' + (xy')'' + (z)'' \\ &= ((x'y)' (xy)') (z)' \\ &= F5 \end{aligned}$$

(3) 2 種方法

$$\begin{aligned} (a) \quad (F4)' &= (x'y'z' + xyz)' \\ F4 &= (x'y'z' + xyz)' = (x+y+z)(x'+y'+z)' \\ &= ((x+y+z)(x'+y'+z))' \\ &= F6 \end{aligned}$$

(b) 已知  $(AB)' = (A'+B)'$  :

所以由  $F5$  可以得:

$$\begin{aligned} ((x'y)' (xy)') (z)' &= ((x+y)' (x'+y) (z)')' \\ &= F6 \end{aligned}$$

```

timescale 1ns / 1ps

module exercise_3(F4,F5,F6,x,y,z);
    output F4,F5,F6;
    input x,y,z;
    wire not_x,not_y,not_z,n1,n2,n3,n4;

    not(not_x,x);
    not(not_y,y);
    not(not_z,z);


    and(n1,not_x,y);
    and(n2,x,not_y);
    or(F4,n1,n2,z);

    nand(n3,not_x,y);
    nand(n4,x,not_y);
    nand(F5,n3,n4,not_z);

    or(n5,x,y,z);
    or(n6,not_x,not_y,z);
    nand(n7,n5,n6);
    not(F6,n7);

endmodule
    
```



 

由電壓圖 F4=F5=F6(上到下: 輸入:x,y,z 輸出:F4,F5,F6 )

#### 四、Exercise 4:

■ Simplify the following Boolean function using Karnaugh maps:  
 $F(x,y,z) = \Sigma (1,2,3,4,5,7)$

■ Find the simplest product of sums (F7) and draw its logic diagram (two-level implementation)

- ◆ Implement F7 with two-level NOR gate circuit (denoted as F8)
- ◆ Implement F7 with two-level AND-NOR (AOI) circuit (denoted as F9)
- ◆ Verify  $F7 = F8 = F9$  (using Verilog Structural level modeling)

		y			
		00	01	11	10
x	0	0	1	1	1
	1	1	1	1	0

程式碼如右:

(1)  $F7' = (x'y'z' + xyz')$

$F7 = (x'y'z' + xyz')' = (x+y+z)(x'+y'+z)$

(2)  $F7 = (x+y+z)(x'+y'+z)$

$= ((x+y+z)' + (x'+y'+z)')$   
 $= F8$

(3) 2 種方法

(a)  $F7 = F4 = x'y + xy' + z$   
 $x'y + xy' + z = ((x'y + xy' + z)')$   
 $= F9$

(b) 已知  $(A+B)' = (A'B)'$ :  
 所以由 F8 可以得:  
 $((x+y+z)' + (x'+y'+z)')$   
 $= ((x'y'z') + (xyz'))'$   
 $= F9$

```

timescale 1ns / 1ps

module exercise_4(F7,F8,F9,x,y,z);
    output F7,F8,F9;
    input x,y,z;
    wire not_x,not_y,not_z,n1,n2,n3,n4,


    not(not_x,x);
    not(not_y,y);
    not(not_z,z);

    or(n1,x,y,z);
    or(n2,not_x,not_y,z);
    and(F7,n1,n2);

    nor(n3,x,y,z);
    nor(n4,not_x,not_y,z);
    nor(F8,n3,n4);

    and(n5,not_x,y);
    and(n6,x,not_y);
    nor(n7,n5,n6,z);
    not(F9,n7);

endmodule
    
```

 

由電壓圖 F7=F8=F9(上到下: 輸入:x,y,z 輸出:F7,F8,F9 )

# 實驗心得

1. Structural level modeling 中邏輯閘使用函數表示
  2. Structural level modeling 可以很直觀的轉換成 Schematic
  3. Structural level modeling 需要宣告邏輯閘之間的線路
  4. 所有的 modeling 都需要注意該邏輯閘是否有交換律或結合律
  5. Exercise 1 的 don't care conditions 很好用可以簡化電路
  6. Exercise 2、3、4 電路的轉換用 Schematic 畫出來後比較簡單。
- 例如:exercise2:AND-OR gate 轉成 multi-level NAND gate、multi-level NOR gate.....。