

Exercise 1:

Exercise 1: 4-bit by 4-bit Binary Multiplier

- Design and verify the 4-bit by 4-bit binary multiplier

Exercise 2:

Exercise 2: 8-bit Magnitude Comparator (1/2)

- Design and verify the 8-bit magnitude comparator composed of two 4-bit magnitude comparators
-

實驗內容

一、Exercise 1:

Exercise 1: 4-bit by 4-bit Binary Multiplier

■ Design and verify the 4-bit by 4-bit binary multiplier


```
1 : `timescale 1ns / 1ps
2 : module half_adder (output S, C, input x, y);
3 :   xor (S, x, y);
4 :   and (C, x, y);
5 : endmodule
6 :
7 : module full_adder (output S, C, input x, y, z);
8 :   wire S1, C1, C2;
9 :   half_adder HA1 (S1, C1, x, y);
10 :   half_adder HA2 (S, C2, S1, z);
11 :   or (C, C2, C1);
12 : endmodule
13 :
14 : module multiplier (output [3:0]M, input [3:0]A, input B);
15 :   and (M[0], A[0], B);
16 :   and (M[1], A[1], B);
17 :   and (M[2], A[2], B);
18 :   and (M[3], A[3], B);
19 : endmodule
20 :
21 : module full_adder_4_number (output S, Cout1, Cout2, Cout3, input A, B, C, D, Cin1, Cin2, Cin3);
22 :   wire half_sum1, half_sum2, half_sum3;
23 :
24 :   full_adder FA0 (half_sum1, Cout1, Cin1, Cin2, Cin3);
25 :   full_adder FA1 (half_sum2, Cout2, A, B, C);
26 :   full_adder FA (S, Cout3, D, half_sum1, half_sum2);
27 :
28 : endmodule
29 :
30 : module exercise_1 ( output [7: 0] Sum, output C8, input [3:0] A, B, input C0);
31 :   wire C1, C2, C3, C4, C5, C6, C7, C8, C9, C10, C11, C12, C13, C14, C15, C16, C17; // Intermediate carries
32 :   wire [3:0]M0;
33 :   wire [3:0]M1;
34 :   wire [3:0]M2;
35 :   wire [3:0]M3;
36 :   multiplier multiplier0(M0, A, B[0]);
37 :   multiplier multiplier1(M1, A, B[1]);
38 :   multiplier multiplier2(M2, A, B[2]);
39 :   multiplier multiplier3(M3, A, B[3]);
40 :
41 :   full_adder FA0 (Sum[0], C1, M0[0], 1'b0, C0);
42 :   full_adder FA1 (Sum[1], C2, M1[0], M0[1], C1);
43 :
44 :   full_adder_4_number FA4_2(Sum[2], C3, C4, C5, M2[0], M1[1], M0[2], 1'b0, C2, 1'b0, 1'b0);
45 :   full_adder_4_number FA4_3(Sum[3], C6, C7, C8, M3[0], M2[1], M1[2], M0[3], C3, C4, C5);
46 :   full_adder_4_number FA4_4(Sum[4], C9, C10, C11, M3[1], M2[2], M1[3], 1'b0, C6, C7, C8);
47 :   full_adder_4_number FA4_5(Sum[5], C12, C13, C14, M3[2], M2[3], 1'b0, 1'b0, C9, C10, C11);
48 :   full_adder_4_number FA4_6(Sum[6], C15, C16, C17, M3[3], 1'b0, 1'b0, 1'b0, C12, C13, C14);
49 :
50 :   full_adder FA7 (Sum[7], C8, C15, C16, C17);
51 :
52 : endmodule
53 :
54 :
55 :
56 :
57 :
58 :
59 :
60 :
61 :
62 :
63 :
64 :
65 :
66 :
67 :
68 :
69 :
70 :
71 :
72 :
73 :
74 :
75 :
76 :
77 :
78 :
79 :
80 :
81 :
82 :
83 :
84 :
85 :
86 :
87 :
88 :
89 :
90 :
91 :
92 :
93 :
94 :
95 :
96 :
97 :
98 :
99 :
100 :
```

4 位元乘法中，最多會有 7 個 input 要相加，7 個 input 用 3 個 full

adder 最多會產生 3 個進位，所以最多會有 7 個 input

$$9 \times 7 = 63 = 00111111_2$$

$$10 \times 14 = 140 = 10001100_2$$

 

二、Exercise 2:

```

1  timescale 1ns / 1ps
2  module xi (output x, input A, B);
3      wire n1;
4      xor (n1, A, B);
5      assign x=~n1;
6  endmodule
7
8  module Gi (output G, input [3:0]A, B);
9      wire x0,x1,x2,x3;
10     xi x_0(x0,A[0],B[0]),
11     x_1(x1,A[1],B[1]),
12     x_2(x2,A[2],B[2]),
13     x_3(x3,A[3],B[3]);
14     assign G=(A[3]&~B[3]) | (x3&A[2]&~B[2]) | (x3&x2&A[1]&~B[1]) | (x3&x2&x1&A[0]&~B[0]);
15 endmodule
16
17 module Li (output L, input [3:0]A, B);
18     wire x0,x1,x2,x3;
19     xi x_0(x0,A[0],B[0]),
20     x_1(x1,A[1],B[1]),
21     x_2(x2,A[2],B[2]),
22     x_3(x3,A[3],B[3]);
23     assign L=(B[3]&~A[3]) | (x3&B[2]&~A[2]) | (x3&x2&B[1]&~A[1]) | (x3&x2&x1&B[0]&~A[0]);
24 endmodule
25
26 module Ei (output E, input [3:0]A, B);
27     wire x0,x1,x2,x3;
28     xi x_0(x0,A[0],B[0]),
29     x_1(x1,A[1],B[1]),
30     x_2(x2,A[2],B[2]),
31     x_3(x3,A[3],B[3]);
32     assign E=x3&x2&x1&x0;
33 endmodule
34
35 module Magnitude_Comparator_4_bit ( output E, L, G, input [3:0] A, B);
36     Ei E1(E,A[3:0],B[3:0]);
37     Gi G1(G,A[3:0],B[3:0]);
38     Li L1(L,A[3:0],B[3:0]);
39 endmodule
40
41 module exercise_2 ( output E, L, G, input [7:0] A, B);
42     wire E1,E2,G1,G2,L1,L2;
43     Magnitude_Comparator_4_bit MC4_1 ( E1, L1, G1, A[7:4], B[7:4]);
44     Magnitude_Comparator_4_bit MC4_2 ( E2, L2, G2, A[3:0], B[3:0]);
45     assign E=(E1&E2);
46     assign G=G1|(E1&G2);
47     assign L=L1|(E1&L2);
48
49 endmodule

```

8bit 比較器拆成 2 個 4bit 比較器

4bit 比較器拆成 L、G、E 3 個小 module

L、G、E 3 個 module 提出共同 module :x


10101010, 10101010

11010011, 10100000

01010111, 01010011

01111111, 10000000

10010011, 10010100

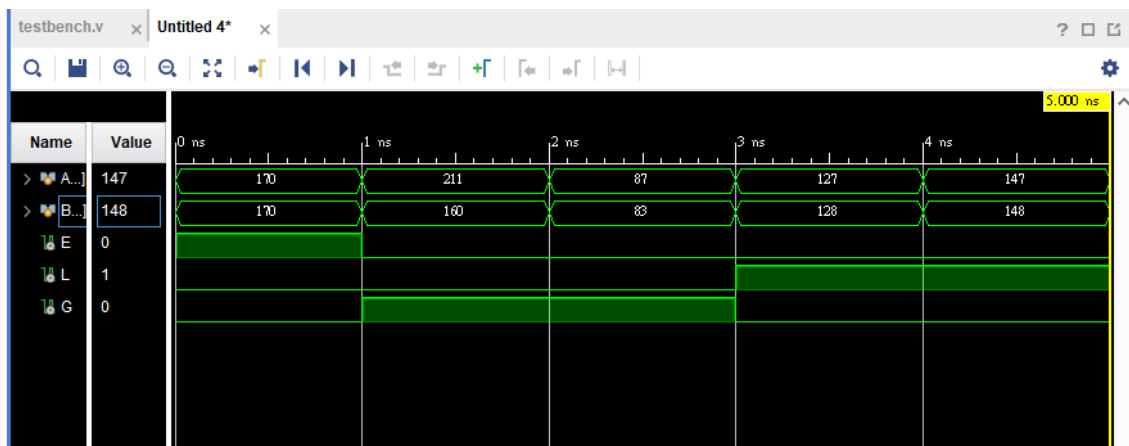

實驗心得

1. Structural level modeling 中邏輯閘使用函數表示
2. Structural level modeling 可以很直觀的轉換成 Schematic
3. Structural level modeling 需要宣告邏輯閘之間的線路
4. 所有的 modeling 都需要注意該邏輯閘是否有交換律或結合律